

13.15 MULTIPLE CHOICE QUESTIONS (SELF PRACTICE):

Electric Current:

- Q.1 An electric current is caused by the motion of:
 * Electric discharge ✓ Electric charge
 * Volt * None of these
- Q.2 The rate of transfer of charges through a circuit is called: (2006)
 * Resistance ✓ Current
 * Potential difference * All of these
- Q.3 Electrical conductors contain: (2003 P.E)
 * Only free electrons * Only bound electrons
 ✓ Both free and bound electrons * Neither bound nor free electrons
- Q.4 If a net charge Q passes through any cross section of a conductor in time t , then the electric current established through the conductor is $I =$
 ✓ $\frac{Q}{t}$ * $\frac{t}{Q}$ * $\frac{1}{Qt}$ * Qt
- Q.5 The S.I unit of current is:
 * Electron volt * Volt ✓ Ampere * Voltage
- Q.6 The current due to flow of charge at the rate of one coulomb per second is called:
 * Electron volt * Volt ✓ Ampere * Voltage
- Q.7 Charge carrier in Metallic conductors are the electrons of:
 ✓ Valence shells * All shells * Excited states * Inner shells
- Q.8 Free electrons in an Electric field moves from:
 * All potentials * High Potential to low potential
 ✓ Low potential to high potential * None of these
- Q.9 The drift velocity is of the order of:
 * 10^5 ms^{-1} * 10^3 ms^{-1} * 10^2 ms^{-1} ✓ 10^{-3} ms^{-1}
- Q.10 2.0×10^8 electrons pass through a conductor in $5.0 \mu\text{s}$. Electronic charge is 1.6×10^{-19} . The current in ampere following through the conductor is:
 * $1.6 \times 10^{-6} \text{ A}$ * $2.6 \times 10^{-6} \text{ A}$ * $3.6 \times 10^{-6} \text{ A}$ ✓ $6.4 \times 10^{-6} \text{ A}$
- Q.11 Which of the following represents an electric current:
 * Erg C^{-1} ✓ C S^{-1} * J S^{-1} * Dyne S^{-1}
- Q.12 If 1 ampere current flows 2m long conductor, the charge flow through this in 1 hour will be:
 ✓ 3600 C * 7200 C * 1 C * 2 C

Ohm's Law:

- Q.13 The current flowing through a conductor is directly proportional to the potential difference across its ends provided the physical state of the conductor remains constant this is:
 * Newton's Law * Coulomb's Law
 * Maxwell's Law ✓ Ohm's Law
- Q.14 Symbolically Ohm's Law can be written as:
 * $I \propto \frac{1}{\sqrt{V}}$ * $I \propto \sqrt{V}$ * $I \propto \frac{1}{V}$ ✓ $I \propto V$
- Q.15 In the relation $I = KV$, K stands for:
 ✓ Conductance * Resistivity
 * Specific Resistance * Permeability

Q.16 Ohm's Law is obeyed in:

- * A semiconductor
- * An electron tube

* A metallic conductor

In all of these

(2003 P.E)

Q.17 The graphical representation of Ohm's Law is:

- * Hyperbola
- * Ellipse

* Parabola

Straight Line

Q.18 If R is the resistance of the conductor, then Ohm's Law can be written as:

* $V = \frac{R}{\sqrt{I}}$

* $V = \frac{R}{I}$

* $V = \frac{I}{R}$

$V = IR$

Resistance and Resistivity:

Q.19 The measure of the opposition to the motion of electrons due to their continuous bumping with the atom of the lattice is the:

Resistance

* Friction

* Voltage

* Work

Q.20 The S.I unit of resistance:

* Volt

* Ampere

* mho

Ohm

Q.21 If a current of 1 ampere flows through a conductor where a potential difference of 1 volt is applied across its ends, then resistance of the conductor is:

* 0 Ohm

1 Ohm

* 2 Ohm

* 3 Ohm

Q.22 The symbols of Ohm is:

* α

* β

* γ

Ω

Q.23 A sample of conductor is said to obey Ohm's Law if its resistance R:

* Increases

* Decreases

Remains constant

* None of these

$V \propto I$

Q.24 Resistance of conductor depends upon:

* The potential difference between its ends

* The magnitude of the current flowing through it

* The nature only

The nature, dimension and physical state of the conductor

Q.25 A wire of length L and resistance R is cut into four equal pieces. Resistance of each piece would be:

* R

* $\frac{R}{2}$

* 2R

$\frac{R}{4}$

Q.26 The resistance of a conductor of length L, cross-sectional area A and resistivity ρ is given by:

* $R = \rho A/L$

$R = \rho \frac{L}{A}$

* $R = \frac{\rho}{LA}$

* $R = \frac{A}{\rho L}$

Q.27 A piece of wire of length "L" and an area of cross-section "A" has a resistance "R". Another piece of wire of the same material and the same length but twice the area of cross-section is connected end-to-end with the previous wire. The effective resistance is:

* R

* 2R

$1/3R$

* $1/2R$

Q.28 Volt per Ampere is:

Ohm

* Joule

* Watt

* KWh

Q.29 The reciprocal of the resistance of conductor is called:

* Specific resistance

* Current

Conductance

* Voltage

Q.30 The unit of conductance is:

* Ohm

* Metre

* Ampere

mho or siemens

- Q.31 The resistance of a meter cube of the substance is called:
 * Conductivity * Permittivity Resistivity * Susceptibility
- Q.32 The resistivity of the material having the resistance R cross-sectional area A and length L is given by:
 * $\rho = \frac{AL}{R}$ * $\rho = RAL$ $\rho = \frac{RA}{L}$ * $\rho = \frac{L}{RA}$
- Q.33 The S.I unit of resistivity is:
 * Ohm - m⁻² Ohm - m⁻¹ Ohm - m * Ohm
- Q.34 A copper wire having resistivity "ρ" is stretched in such a way that its diameter reduces to half of that of the original wire. The new resistivity will be:
 * Halved * Doubled The same * Four fold
- Q.35 A wire of a uniform cross-section area is cut into three equal segments. The resistivity "ρ" of each segment will be:
 * 1/3ρ * 2/3ρ
 Same as that of the whole wire * Three times as that of the whole wire
- Q.36 If the wire of a uniform area of cross section is cut into two equal parts, the resistivity of each part will be:
 * Halved * Doubled
 Remains the same * None of the above
- Q.37 Resistance of a substance one meter in length and one square meter in cross sectional area is called:
 * Conductivity Resistivity * Permittivity * Reactance
- Q.38 When the temperature of a conductor is raised its resistance:
 Always decreases Always increases
 * Remains the same * First increases and then decreases
- Q.39 The resistance of the conductor increases due to the rise of temperature of a conductor, because the collision cross section of the atoms:
 * Decreases Increases
 * Remains unchanged * sometime increases and sometime decreases
- Q.40 The temperature co-efficient of resistivity of a material is given by the relation:
 * $\alpha = \rho \Delta T / \rho_T - \rho_0$ $\alpha = \frac{(\rho_T - \rho_0)}{\rho_0 \Delta T}$
 * $\alpha = \rho_0 (\rho_T - \rho_0) / \Delta T$ * $\alpha = \Delta T (\rho_T - \rho_0) \rho_0$
- Q.41 The temperature co-efficient of resistance of a material is given by the relation:
 $\alpha = \frac{(R_T - R_0)}{R_0 \Delta T}$ * $\alpha = \frac{R_0 \Delta T}{(R_T - R_0)}$
 * $\alpha = \frac{R_0}{(R_T - R_0) \Delta T}$ * $\alpha = \frac{\Delta T (R_T - R_0)}{R_0}$
- Q.42 The S.I unit of the temperature co-efficient of resistivity of material is:
 * Ohm - m * K K⁻¹ * Ohm - K

Resistance in Series:

- Q.43 If the resistance are connected end to end such that the same current passes through all of them, then they are said to be connected:
 * Parallel Series
 * Not in Series * Neither in Series nor parallel

Q.44 If equivalent resistance R of the resistance R_1, R_2, R_3 is series is $R =$:

* $\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ * $\frac{R_1 + R_2 + R_3}{R_1 R_2 R_3}$ * $R_1 + R_2 + R_3$ * $R_1 R_2 R_3$

Q.45 The potential difference across each resistance in series combination is:

- * Same * Different * Infinity * Zero

Q.46 When the resistance are connected in series, the equivalent resistance is always:

- * Greater than the greatest resistance in series
 * Equal to the greatest resistance in series
 * Less than the largest resistance in series
 * Less than the smallest resistance in series

Q.47 When the resistors are connected in series then:

- * The total current through each is the same
 * The voltage across each is the same
 * The total resistance is the sum of the reciprocals of the individual
 * The total resistance is the product of the individual resistors

Q.48 Resistors of 2 ohm, 3 ohm, 4 ohm and 5 ohm are connected in series. If the current through the 2 ohm resistor is one ampere the current through the other resistors will be:


- * 4 ampere * 1 ampere * 14 ampere * 0.1 ampere

Q.49 A piece of wire of length "L" and an area of cross-section "A" has a resistance "R". Another piece of wire of the same material and the same length but twice the area of cross-section is connected end-to-end with the previous wire. The effective resistance is:

- * R * 2R * $\frac{1}{3}R$ * $\frac{1}{2}R$

Q.50 If Net resistance of resistors increases, then resistors are in:

- * Parallel combination * Series Combination
 * Simultaneously in series and in parallel combination
 * Either in series or in parallel combination

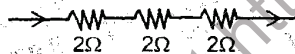Q.51 

In the figure above the equivalent resistance is:

- * 3 Ω * 6 Ω * 4 Ω * 2 Ω

Q.52 Three resistance 5000, 500, 50 ohm are connected in series across 555 volt mains. The current flowing through them will be:

- * 1 A * 100 mA * 10 mA * 10 A

Resistance in Parallel:

Q.53 If the resistors are connected side by side with their ends joined together at common point, then they are said to be connected:

- * Parallel * Series
 * Not Parallel * Neither in Series nor parallel

Q.54 The equivalent resistance R of the resistance R_1, R_2, R_3 connected parallel is R :

* $\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$ * $\frac{R_1 + R_2 + R_3}{R_1 R_2 R_3}$ * $R_1 + R_2 + R_3$ * $R_1 R_2 R_3$

Q.55 The potential difference across each resistance are connected in parallel combination:

- * Same * Different * Infinity * Zero

- Q.56 When the resistance are connected in parallel, the equivalent resistance is always:
- * Greater than the sum of the individual resistance
 - * Greater than the smallest resistance in combination
 - * Equal to the sum of the individual resistance
 - Less than the smallest resistance in the combination

Q.57 In a house circuit all the electrical appliances are connected in parallel with the phase and the neutral to get:

- The same current and different potential difference
- The different currents but the same potential difference
- * The different currents and different potential differences
- * The same current and the same potential difference

Q.58 The resistances of 2 ohms, 5 ohms, 7 ohms and 9 ohms are connected in parallel. If the potential difference across the 5 ohms resistance is 5V, the potential difference across 9 ohm resistance will be:


- * 9V
- 5V
- * 2.5V
- * 1.5V

Q.58(a) Resistors of 3Ω, 5Ω and 7Ω are connected in parallel. If the P.D across 5Ω resistor is 6V, the P.D across the other resistors is: (2013)

- * 4 Volt
- 6 Volt
- * 8 Volt
- * 10 Volt

Q.59 Three resistors of resistance 2, 3 and 6 ohms are connected in parallel, their equivalent resistance is:

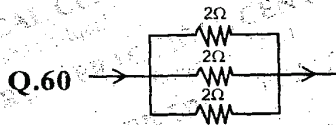- * 11.0 ohm
- * 1.33 ohm
- * 1.5 ohm
- * 1.0 ohm



If the figure above the equivalence is: $\frac{2}{3}\Omega$ * $\frac{3}{2}\Omega$ * $\frac{1}{3}\Omega$ * 6Ω

Power Dissipation in Resistance:

Q.61 As the charge flows through the conductor energy is dissipated in the form of:

- Heat
- * Solar energy
- * Light
- * None of these

Q.62 One-Kilo-Watt-Hour is equal to:

- $3.6 \times 10^5 \text{J}$
- * $360 \times 10^6 \text{J}$
- * $3.6 \times 10^4 \text{J}$
- * $36 \times 10^5 \text{J}$

Q.63 The power dissipated by a resistance is given by:

- * $P = VR$
- $P = V^2/R$
- * $P = IR^2$
- * None of these

Q.64 The power dissipated in a resistance is given by:

- IV
- I^2R
- V^2/R
- All of these

Q.65 The electrical energy dissipated as heat in a resistor is given by:

- * I^2R
- I^2Rt
- * V^2R
- * V^2Rt

Q.66 The commercial unit of electrical energy is:

- * Ohm
- Watt
- Kilowatt-Hour
- * Ampere

Q.67 Two wires of resistance R_1 and R_2 are connected in series in a circuit. If R_1 is the greater than R_2 , Heating would be:

- More in R_1
- * More in R_2
- * Same in R_1 & R_2
- * All of these

Q.68 When a resistor carries a current "I", the power dissipated by it is "P". If the same resistor carries the current of "3I", the power dissipated will be:

- * P
- * P/3
- 3P
- * None of the above

Q.69 Unit of Power, Joule / Second is called:

- * Joule
- * Volt
- Watt
- * Newton

Q.70 If one ampere current flows through a resistor against potential difference of one volt, this is called:

- * Ampere
- Watt
- * Volt
- * Joule

- Q.71 The practical unit power is:
 * Watt Kilowatt * Joule * None of these
- Q.72 One Kilowatt is equal to:
 * 10^5 Watt * 10^6 Watt 10^3 Watt * None of these
- Q.73 Amount of energy delivered by the current in one hour when it supplies energy at the rate of 1000 J/S is known as:
 * Joule kWh * Newton * None of these
- Q.74 Which one of the following bulbs has least resistance?
 * 100 Watt * 200 Watt 500 Watt * 60 Watt
- Q.75 If a 40 watt light bulb for 2 hour, how much heat is generated?
 * 80 J * 400 J * 288×10^3 J * 3600 J
- Q.76 The resistance of 60 watt bulb is a 120 volt line is:
 * 30 ohm * 120 ohm * 240 ohm * 60 ohm

Electromotive Force:

- Q.77 The work per unit charge done by the source in moving a charge around a closed loop is called:
 Electromotive force * Potential difference
 * Potential energy * Kinetic energy
- Q.78 The total energy expended per coulomb of electricity when charge is driven round a circuit is called:
 Electromotive force * Electromotive source
 * Potential energy * Kinetic energy
- Q.79 The unit of electromotive force is:
 * Coulomb per second * Joule per second
 Joule per coulomb * Volt per ampere
- Q.80 By electromotive force:
 * Light is produced * Heat is produced
 Current is produced * Sound is produced
- Q.81 The terminal potential difference V_t of a battery is always:
 * Equal to emf of the battery Less than emf of battery
 * Greater than the emf of battery * Zero
- Q.82 Internal resistance is the resistance offered by:
 Source of emf * The conductor * The circuit * The resistance
- Q.83 Terminal potential difference V_t of a battery of internal resistance ' γ ' and emf 'E' is:
 (2011 Supp.)
 * $V_t = E + Ir$ $V_t = E - Ir$ * $V_t = EIr$ * $V_t = E \frac{r}{I}$
- Q.84 The emf of a source is equal to the potential difference across the terminals of the source when its internal resistance is:
 (2001)
 Zero * Very high * Very low * None of these
- Q.85 The E.M.F. of the three cells, each of 2 volts, in parallel will be:
 * 6V * 8V 2V * Zero V
- Q.86 Total potential difference across the combination of three cells becomes maximum when:
 (2003 P.M.)
 All the three cells are connected in series
 * All the three cells are connected in parallel
 * Two cells are connected in parallel and the third cell in series with the combination.
 * Two cells are connected in series and the third cell in parallel with the combination.

ANSWER KEY

1. Electric Charge	2. Current
3. Both free and bound electrons	4. $\frac{\theta}{l}$
5. Ampere	6. Ampere
7. Valence shells	8. Low potential to high potential
9. 10^{-3} m/s	10. 6.4×10^{-6} A
11. CS^{-1}	12. 3600 C
13. Ohm's Law	14. $I \propto V$
15. Conductance	16. In all of these
17. Straight Line	18. $V = IR$
19. Resistance	20. Ohm
21. 1 Ohm	22. Ω
23. Remains Constant	24. The nature dimension and physical state of the conductor
25. $R/4$	26. $R \propto \rho \frac{L}{A}$
27. $1/3 R$	28. Ohm
29. Conductance	30. mho or semen
31. Resistivity	32. $\rho = \frac{RA}{L}$
33. Ohm - m	34. The same
35. Same as that of the whole wire	36. Remains the same
37. Resistivity	38. Always increases
39. Increases	40. $\alpha = \frac{(\rho_t - \rho_o)}{\rho_o \Delta T}$
41. $\alpha = \frac{R_t - R_o}{R_o \Delta T}$	42. K^{-1}
43. Series	44. $R_1 + R_2 + R_3$
45. Different	46. Greater than the greatest resistance in series
47. The total current through each is the same	48. 1 ampere
49. $\frac{1}{3} R$	50. Series Combination
51. 6Ω	52. 10 A
53. Parallel	54. $\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
55. Same	56. Less than the smallest resistance in combination
57. The different current but same potential difference	58. 5 V 58(a). 6 V
59. 1.0 ohm	60. $\frac{2}{3}$
61. Heat	62. 36×10^5 J
63. $P = V^2/R$	64. All of these
65. $I^2 Rt$	66. Kilowatt Hour
67. More in R_1	68. 3 P
69. Watt	70. Watt
71. Kilowatt	72. 10^3 Watt
73. KWh	74. 500 Watt
75. 288×10^3 J	76. 240 ohms
77. Electromotive Force	78. Electromotive Force
79. Joule per coulomb	80. Current is produced
81. Less than emf of battery	82. Source of emf
83. $V_t = E - I_r$	84. Zero
85. 2V	86. All the three cells are connected in series

15.14 MULTIPLE CHOICE QUESTIONS (SELF PRACTICE):

Galvanometer:

- (1) An device used for the detection and measurement of current is called:
* Galvanometer * Voltmeter * Ammeter * Avometer
- (2) The working of a galvanometer depends upon the:
* Force exerted on the coil * Torque exerted on the coil
* Mass of the coil * Area of coil
- (3) Galvanometer is based on the:
* Electromagnetic effect of current * Chemical effect of current
* Magnetic effect of current * Heating effect of current
- (4) The current passing through the coil of the galvanometer is:
* Inversely proportional to the angle of deflection of the coil
* Independent of the coil
* Directly proportional to the angle of deflection of the coil
* None of the above
- (5) The galvanometer constant is given by:
* C/NAB * NAB/C * NAC/B * NB/AC
- (6) The galvanometer can be made sensitive by making the value of factor C/NAB :
* Large * Small * Zero * Infinite
- (7) The sensitivity of a galvanometer can be increased by increasing: (2008)
* Magnetic field * Area of coil * Number of turns * All of them
- (8) $I = \frac{C}{BNA} \theta$ Hence to increase the sensitivity of a galvanometer, we must decrease the value of:
* θ * N * B * C
- (9) The unit of least count on a galvanometer scale represents:
* Division * Ohm * Volt * Henry
- (10) When the coil of the galvanometer in equilibrium, then the deflecting couple is:
* Zero * Equal to the restoring couple
* Greater than the restoring couple * Smaller than the restoring couple

Ammeter:

- (11) A device which is used to measurement of current is called:
* Ammeter * Voltmeter * Galvanometer * Avometer
- (12) A galvanometer is converted into an ammeter by connecting a suitable:
* High resistance in series * Low resistance in parallel
* High resistance in parallel * Low resistance in series

(2008, 2003 P.E, 2002 P.E, 2001)

(13) To convert a galvanometer into an ammeter the shunt resistance is given by:

$$* R_s = \frac{I_g R_g}{I - I_g} \quad * R_s = \frac{I_g R_g}{I - I_g} \quad * R_s = \frac{I - I_g}{I_g} R_g \quad * \frac{I - I_g}{I_g R_g}$$

(14) In order to increase the range of ammeter the shunt resistance is:

- * Decreased
- * Increased
- * Kept constant
- * Sometimes increased and sometime decreased

(15) In a circuit Ammeter is always connected in:

- * Series
- * Parallel
- * Both series and parallel
- * None of these

(16) A good ammeter is one which:

- * Can measure both alternating and direct current
- * Has very small internal resistance
- * Has very high internal resistance
- * Has linear scale of measurement

(17) A device which is used to measurement of voltage is called:

- * Ammeter
- * Voltmeter
- * Galvanometer
- * Avometer

(18) To convert a galvanometer into a voltmeter a resistance is connected in:

- * High resistance in series
- * Low resistance in parallel
- * High resistance in parallel
- * Low resistance in series

(19) To convert a galvanometer into a voltmeter the high resistance is given by:

$$* R_x = \frac{R_g - V}{(I - I_g)} \quad * R_x = \frac{I - I_g}{I_g R_g} \quad * R_x = \frac{V}{I_g} - R_g \quad * R_x = R_g \frac{V}{I_g}$$

(20) In order to increase the range of voltmeter the high resistance is:

- * Decreased
- * Increased
- * Kept constant
- * Sometime increased and some time decreased

(21) In a circuit, voltmeter is always connected in:

- * Series
- * Parallel
- * Both series and parallel
- * None of these

(22) A good voltmeter is one which:

- * Can measure both A.C and D.C
- * Has linear side of measurement
- * Has very small internal resistance
- * Has very high internal resistance

Wheatstone Bridge:

(23) A balanced Wheatstone bridge is used to measure:

- * Current
- * Voltage
- * Unknown resistance
- * Electric flux

(24) When Wheatstone bridge is balanced then:

- * Galvanometer is giving full deflection
- * Galvanometer's deflection is zero
- * $R_1 / R_2 > R_3 / R_4$
- * $R_1 / R_3 < R_3 / R_2$

- (25) Wheatstone bridge is an arrangement consisting of:
 * Three resistances * Two resistances * Four resistances * Five resistances
- (26) The condition for the Wheatstone Bridge to be balanced is given by:
 * $\frac{R_1}{R_2} = \frac{R_4}{R_3}$ * $\frac{R_1}{R_2} = \frac{R_3}{R_4}$ * $\frac{R_2}{R_1} = \frac{R_3}{R_4}$ * $\frac{R_2}{R_1} = \frac{R_4}{R_3}$
- (27) In a Wheatstone Bridge circuit we balance:
 * Resistance * Current * Voltage * All of these
- (28) Balanced position of wheatstone bridge is obtained when potential at the terminals of Galvanometer:
 * is same * is altered * is different * is established
- (29) A meter bridge is an apparatus used to measure the: (2013)
 * Current * Voltage * Magnetic field * Unknown resistance
- (30) A meter bridge also called:
 * Voltmeter * Ammeter * Galvanometer * Slide-wire bridge
- (31) The construction of meter bridge is based on the principle of a:
 * Voltmeter * Ammeter * A.C generator * Wheatstone bridge
- (32) Slide-wire bridge is a practical form of the:
 * Galvanometer * Post office box * Voltmeter * Wheatstone bridge
- (33) In Slide-wire bridge method, the unknown resistance is determined by the relation:
 * $x = \frac{\ell_2}{\ell_1} R$ * $x = \frac{1}{\ell_2} R$ * $x = \frac{R}{\ell_1 \ell_2}$ * $x = \frac{\ell_1}{\ell_2 R}$

Post Office Box:

- (34) P.O. Box is used to find:
 * Current * Resistance * e.m.f. * All of these
- (35) The working principle of a post office box is:
 * Wheatstone Bridge * Potentiometer * Telegraph line * None of these
- (36) Post office is a practical form of:
 * Ammeter * Voltmeter * Meter bridge * Wheatstone bridge
- (37) Which one of the following instrument can measure the unknown resistance which sufficient accuracy?
 * Potentiometer * Slide wire bridge * Post office box * Galvanometer
- (38) Three arms of a balanced post office box are 75 ohm resistance each. What is the resistance of the fourth arm?
 * 225 ohm * 150 ohm * 75 ohm * 300 ohm

Potentiometer, Ohmmeter, Avometer:

- (39) A potentiometer is an instrument used to measure:
 * Current * Voltage * Resistance * Electric flux

- (40) An instrument which measures potential without drawing any current from the circuit is known as:
* Voltmeter * Avometer * Potentiometer * Galvanometer
- (41) A potentiometer circuit give continuously varying:
* Potential difference * Capacitance
* Charge * Inductance
- (42) The apparatus used to compare the emf of two cell is:
* A Wheatstone bridge * A galvanometer
* A potentiometer * A ammeter
- (43) Which one of the following is used to determine internal resistance of a cell?
* Ammeter * Voltmeter * Galvanometer * Potentiometer
- (44) Potentiometer can be used as:
* Ammeter * Voltmeter * Galvanometer * Potential divider
- (45) Potentiometer is used to: (2003 P.M)
* Compare emf of two cell * Detect internal resistance of cell
* Measure P.D * All of these
- (46) To increase the accuracy of potentiometer: (2011, 2003 P.E)
* A uniform wire of a large length should be used
* A uniform wire of a small length should be used
* A non uniform wire should be used
* None of these

Miscellaneous:

- (47) An Avometer is a device which can measure: (2012, 2002 P.E)
* Voltage only * Current only
* Resistance only * Current, Voltage and Resistance
- (48) Which of following instruments is used to measure current potential difference and resistance:
* Ammeter * Voltmeter * Galvanometer * Avometer
- (49) A single device containing ammeter voltmeter and ohmmeter is called:
* VTVM * CRO * Potentiometer * Multimeter
- (50) AVO meter is used to find:
* Current * Resistance * e.m.f. * All of these
- (51) Which of the following device is not used for measuring resistance:
* P.O. Box * Potentiometer * Ohmmeter * Meter bridge
- (52) Which of the following can be used to measure the resistance:
* Ohm meter * Meter bridge * P.O Box * All of these

- (53) The process of reducing amplitude of vibration of coil of Galvanometer is called:
* Drifting * Doping * Shunting * Damping
- (54) If the length of the wire of potentiometer is increased, the accuracy in the determination of null point:
* Increases * Decreases * Remains the same * Becomes Zero
- (55) A moving coil galvanometer is converted into an ammeter by connecting to it:
* Low resistance in series * High resistance in series
* High resistance in parallel * Low resistance in parallel
- (56) Galvanometer can be converted into voltmeter by connecting:
* A high resistance in series * A low resistance in series
* A high resistance in parallel * A low resistance in parallel
- (57) Sensitivity of Galvanometer is given by:
* $CBAN$ * $\frac{1}{CBAN}$ * $\frac{C}{BAN}$ * $\frac{BAN}{C}$
- (58) The device which makes use of wheatstone bridge is:
* Meter bridge * Voltmeter * Ohmmeter * Potentiometer
- (59) The device which can measure e.m.f. of cells without drawing current from them is called:
* Potentiometer * Meter bridge * Voltmeter * Ohmmeter
- (60) In a circuit Voltmeter is always connected in:
* Series * Parallel
* Both Series and Parallel * None of these
- (61) To increase the accuracy of a potentiometer:
* A uniform wire of a small length should be used
* Thickness of wire will be increased
* Thickness of wire will be decreased
* A uniform wire of a large length should be used
- (62) The deflection of coil of Galvanometer is directly proportional to:
* Resistance of Coil * Strength of magnetic field
* Current passing through coil * Area of coil
- (63) For Balanced Position of wheatstone bridge:
* $\frac{R_1}{R_3} = \frac{R_2}{R_4}$ * $\frac{R_2}{R_1} = \frac{R_3}{R_4}$ * $R_1R_4 = R_2R_3$ * $R_1R_2 = R_3R_4$

ANSWER KEY

1. Galvanometer	33. $x = \frac{\ell_2}{\ell_1} R$
2. Torque exerted on the coil	34. Resistance
3. Magnetic effect of current	35. Wheatstone bridge
4. Directly proportional to the angle of deflection of the coil	36. Wheatstone bridge
5. C / NAB	37. Post Office Box
6. Small	38. 75 ohm
7. All of them	39. Voltage
8. C	40. Potentiometer
9. Division	41. Potential difference
10. Equal to the restoring couple	42. A potentiometer
11. Ammeter	43. Potentiometer
12. Low resistance in parallel	44. Potential divider
13. $R_s = \frac{I_g R_g}{I - I_g}$	45. All of these
14. Decreased	46. A uniform wire of a large length should be used
15. Series	47. Current, Voltage and Resistance
16. Has very small internal resistance	48. Avometer
17. Voltmeter	49. Multimeter
18. High resistance in series	50. All of these
19. $R_x = \frac{V}{I_g} - R_g$	51. Potentiometer
20. Increased	52. All of these
21. Parallel	53. Damping
22. Has very high internal resistance	54. Increases
23. Unknown resistance	55. Low resistance in parallel.
24. Galvanometer's deflection is zero	56. A high resistance in series
25. Four resistances	57. $\frac{C}{BAN}$
26. $\frac{R_1}{R_2} = \frac{R_3}{R_4}$	58. Meter bridge
27. Voltage	59. Voltmeter
28. Is same	60. Parallel
29. Unknown Resistance	61. A uniform wire of large length
30. Slide-wire bridge	62. Current passing through the coil
31. Wheatstone bridge	63. $R_1 R_4 = R_3 R_2$
32. Wheatstone bridge	